

EE 618 (ZELE)

CMOS Aanlog VLSI Design : Tutorial-I

Note: Consider $V_{DD} = 3\text{V}$, $V_{Tn} = 0.7\text{V}$ and $V_{Tp} = -0.8\text{V}$. Neglect body effect. Assume low frequency small signal model whenever required.

1. Sketch I_X and transconductance ($\frac{\delta I_X}{\delta V_{GS}}$) with respect to V_X for the circuit given in Figure 1, as V_X is swept from 0 to 1.5 V.

 


Figure 1

2. Prove that the structure in Figure 2 can be viewed as a single transistor having aspect ratio ($\frac{W}{2L}$). Assume that $\lambda = \gamma = 0$.

 


Figure 2

3. Sketch I_X versus V_X for the circuit shown in Figure 3, as V_X varies from 0 to V_{DD} .

 


Figure 3

4. Assuming all the transistors are in a saturation, find a small signal voltage gain for the following circuit:

 


Figure 4

5. Assuming all transistors are in a saturation, find a small signal voltage gain for the following circuits:



 


Figure 5 a)

 

b)

 

c)

6. Find the input impedance and transfer function of the circuit in Figure 6. Sketch the gain and phase bode plot.

 


Figure 6